



Table of Contents

Chapter 1 Electrical Fundamentals

Unit 1 Matter	3
Introduction.....	3
1.1 Matter	3
1.2 Atomic Theory.....	3
1.3 Law of Electrical Charges	4
1.4 Law of Atomic Charges.....	4
Negative Atomic Charge.....	4
Positive Atomic Charge	4
1.5 Charged Material (Static Charge)	5
Static Voltage	5
Reducing Static Charge	5
1.6 Neutralizing a Charge	6
1.7 Lightning.....	6
1.8 Lightning Protection	7
Unit 1 – Summary	8
Unit 1 – Conclusion.....	9
Unit 1 – Practice Questions	10
Unit 2 Electron Theory	13
Introduction.....	13
2.1 Electron Orbits	13
2.2 Valence Electrons.....	13
2.3 Freeing Electrons from an Atom.....	13
2.4 Conductors	14
2.5 Insulators	14
2.6 Semiconductors.....	15
2.7 Atomic Bonding	15
2.8 Compounds.....	15
Unit 2 – Summary	16
Unit 2 – Conclusion	17
Unit 2 – Practice Questions	18
Unit 3 Magnetism	21
Introduction.....	21
3.1 The Natural Magnet.....	21
3.2 Magnetic Polarities	21
3.3 Magnetic Compass	21

3.4 Magnetic Molecule	22
3.5 Magnetic Properties.....	22
3.6 How to Magnetize Iron.....	22
3.7 Permanent and Temporary Magnets	22
3.8 Demagnetizing Magnets	22
3.9 Magnetic Lines of Force.....	23
3.10 Magnetic Materials	23
3.11 Law of Attraction and Repulsion	23
3.12 Retentivity.....	23
3.13 Permeability.....	23
Unit 3 – Summary	24
Unit 3 – Conclusion	25
Unit 3 – Practice Questions	26
Unit 4 Electricity	29
Introduction.....	29
4.1 Electrical Current Flow (Electricity).....	29
4.2 Electricity	30
Chemical Activity (Electrochemistry)	30
Magnetism (Magnetoelectricity).....	30
Light (Photoelectricity)	31
Thermo Energy (Thermoelectricity)	32
Pressure (Piezoelectricity)	32
4.3 Useful Purposes of Electricity.....	32
Electrochemistry	32
Electromagnetism.....	33
Heat (Resistance)	33
Illumination Lighting	33
4.4 Danger of Electricity.....	34
Understanding Electrical Shock Hazard	34
What Determines the Severity of Electrical Shock?	35
Clearing a Ground Fault	36
Fire	36
Electrical Arc Blast	36
4.5 National Electrical Code	37
Unit 4 – Summary	38
Unit 4 – Conclusion	40
Unit 4 – Practice Questions	41

Unit 5 Electromagnetism	45	7.7	Power	76
Introduction.....	45	7.8	Electrical Formulas	76
5.1 Electromagnetism in a Wire	45	Unit 7 – Summary	77	
5.2 Field Intensity.....	45	Unit 7 – Conclusion	78	
5.3 Field Interaction	46	Unit 7 – Practice Questions	79	
5.4 Field Interaction of Loops.....	46	Unit 8 Math	81	
5.5 Electromagnetism in a Coil	46	Introduction.....	81	
5.6 Magnetic Core	47	8.1 Whole Numbers	81	
5.7 Ampere and Turns.....	47	8.2 Decimal.....	81	
Unit 5 – Summary	48	8.3 Fractions.....	81	
Unit 5 – Conclusion	49	8.4 Percentages.....	81	
Unit 5 – Practice Questions	50	8.5 Multiplier.....	82	
Unit 6 Uses of Electromagnetism	53	8.6 Percent Increase.....	82	
Introduction.....	53	8.7 Reciprocals	83	
6.1 Basic Electric Meters	53	8.8 Squaring a Number.....	83	
Voltmeter	53	8.9 Square Root	84	
DC Voltmeter.....	54	8.10 Volume.....	85	
DC Ammeter	54	8.11 Kilo.....	85	
Clamp-on AC Ammeter	55	8.12 Rounding Off.....	86	
Ohmmeters.....	55	8.13 Parentheses	86	
Wheatstone Bridge.....	56	8.14 Testing Your Answer for Reasonableness.....	86	
Megohmmeter	56	Unit 8 – Summary	88	
6.2 Electric Motor	57	Unit 8 – Conclusion	89	
Motor Components	57	Unit 8 – Practice Questions	90	
Understanding Motor Motion.....	57	Unit 9 Electrical Formulas	93	
6.3 Electrical Generator.....	58	Introduction.....	93	
DC Generator	58	9.1 Electrical Circuit	93	
AC Generator	58	9.2 Power Source	93	
6.4 Electromagnetic Relay	58	Direct Current	94	
Contacts.....	58	Alternating Current.....	94	
Holding Relay.....	59	9.3 Conductance.....	94	
Unit 6 – Summary	61	9.4 Circuit Resistance	94	
Unit 6 – Conclusion	63	9.5 Ohm’s Law.....	95	
Unit 6 – Practice Questions	64	9.6 Ohm’s Law and Alternating Current	95	
Chapter 1 – Final Review Questions	66	Direct Current	95	
Chapter 2		Alternating Current.....	95	
Basic Electricity		9.7 Ohm’s Law Formula Circle.....	95	
Unit 7 The Electrical Circuit	73	9.8 PIE Formula Circle.....	97	
Introduction.....	73	9.9 Formula Wheel	98	
7.1 The Electrical Circuit	73	9.10 Using the Formula Wheel	98	
7.2 Electron Current Flow Theory.....	74	9.11 Power Losses of Conductors.....	99	
7.3 Conventional Current Flow Theory	74	9.12 Cost of Power	99	
7.4 Voltage (Pressure).....	74	9.13 Power Changes with the Square of the Voltage.....	100	
7.5 Resistance	75	Power Example at 230V.....	100	
Conductor Resistance	75	Power Example at 208V.....	101	
7.6 Electric Current	75	Power Example at 240V.....	101	

Unit 9 – Summary	103
Unit 9 – Conclusion	104
Unit 9 – Practice Questions	105
Chapter 2 – Final Review Questions	108

Chapter 3 Basic Electrical Circuits

Unit 10 Series Circuits	115
Introduction	115
10.1 Practical Uses of the Series Circuit	115
Lighting	115
Control Circuit	116
Signaling Circuit	116
Internal Equipment Wiring	116
10.2 Understanding Series Calculations	116
Resistance	116
Voltage	116
Kirchoff's Voltage Law	117
Kirchoff's Current Law	118
Power	119
10.3 Series Circuit Calculations	119
10.4 Power Calculations	120
10.5 Variations	120
10.6 Series Circuit Notes	120
10.7 Series-Connected Power Supplies	120
Unit 10 – Summary	121
Unit 10 – Conclusion	122
Unit 10 – Practice Questions	123
Unit 11 Parallel Circuits	125
Introduction	125
11.1 Practical Uses	125
Receptacle	125
Lighting	125
Other Uses	125
11.2 Understanding Parallel Calculations	126
Voltage	126
Kirchoff's Current Law	126
Power	127
11.3 Circuit Resistance	127
Equal Resistance Method	128
Product-Over-Sum Method	128
Reciprocal Method	129
11.4 Parallel Circuit Notes	129
11.5 Parallel-Connected Power Supplies	130
Unit 11 – Summary	131
Unit 11 – Conclusion	132
Unit 11 – Practice Questions	133

Unit 12 Series-Parallel Circuits	135
Introduction	135
12.1 Review of Series and Parallel Circuits	135
Series Circuit Review	135
Parallel Circuit Review	135
12.2 Working Series-Parallel Circuits	136
12.3 Voltage	137
12.4 Current	137
Unit 12 – Summary	138
Unit 12 – Conclusion	138
Unit 12 – Practice Questions	139
Unit 13 Multiwire Circuits	141
Introduction	141
13.1 Neutral Conductor	141
13.2 Grounded Conductor	141
13.3 Current Flow on the Grounded (Neutral) Conductor	142
2-Wire Circuit	142
3-Wire 120/240V 1Ø Circuit	142
13.4 Balanced Systems	143
13.5 Unbalanced Current	143
3-Wire 120/240V 1Ø Circuit	143
3-Wire Circuit from a 4-wire 3Ø System	143
4-Wire, 3Ø Circuit	144
13.6 Multiwire Branch Circuit	144
2-Wire Circuit Voltage Drop	144
Multiwire Circuit Voltage Drop	145
13.7 Dangers of Multiwire Circuits	145
Fire Hazard	146
Destruction of Equipment as Well as Fire Hazard	146
13.8 NEC Requirements	147
Unit 13 – Summary	148
Unit 13 – Conclusion	149
Unit 13 – Practice Questions	150
Chapter 3 – Final Review Questions	153

Chapter 4 Electrical Systems and Protection

Unit 14 The Electrical System	159
Introduction	159
14.1 Current Flow	159
14.2 Utility Neutral Current Path	159
Multipoint Neutral Ground	159
14.3 Utility Ground-Fault Current Path	160
14.4 Premises Neutral Current Path	160
Single Point Neutral Bond	160

14.5	Premises Ground-Fault Current Path.....	160	15.12	Neutral-to-Case Detection	177
	Earth as Ground Fault Path for Systems 600V or Less	161	15.13	Line-to-Neutral Shock Hazard.....	177
14.6	Utility High-Voltage Transmission Lines.....	161	15.14	GFCI Fails – Circuit Remains Energized	177
14.7	Conductor Voltage Drop	161	15.15	GFCI Test Button	178
14.8	Conductor Power Loss.....	162	Part C – Arc-Fault Circuit Interrupter.....	178	
	Current.....	162	15.16	Arcing Definition	178
14.9	Reducing Voltage Drop and Power Loss	162	15.17	Series Versus Parallel Arc	179
	138 kV Transmission Line	162		Series Arc	179
14.10	Generating Plants	163		Parallel Arc.....	179
14.11	Step-Up Substation at Generating Plant.....	163	15.18	AFCI and the NEC.....	179
14.12	Transmission Line	163	15.19	AFCI – How They Operate.....	179
14.13	Step-Down Substation.....	163	Part D – Ground-Fault Protection of Equipment.....	180	
14.14	Primary Distribution Feeders.....	163	15.20	Ground-Fault Protection of Equipment Definition	180
14.15	Distribution Transformer.....	164	Unit 15 – Summary	181	
14.16	Secondary Distribution Line	164	Unit 15 – Conclusion	183	
Unit 14 – Summary	165		Unit 15 – Practice Questions	184	
Unit 14 – Conclusion	166		Chapter 4 – Final Review Questions.....	189	
Unit 14 – Practice Questions	167				
Unit 15 Protection Devices.....	171		Chapter 5		
Introduction.....	171		Alternating Current		
Part A – Overcurrent Protection Devices.....	171		Unit 16 Alternating Current.....	195	
15.1	Overcurrent Protection.....	171	Introduction.....	195	
	Overload	171	16.1	Current Flow	195
	Ground Fault	171	16.2	Why Alternating Current is Used	195
	Short Circuit.....	172	16.3	How Alternating Current is Produced	196
15.2	Clearing Faults.....	172	16.4	AC Generator	196
	Time – Current Curves.....	172	16.5	Waveform	197
	Remove Dangerous Touch Voltage.....	172		Direct-Current Waveform	197
15.3	Overcurrent Protection Device Types	172		Alternating-Current Waveform	197
15.4	Fuse.....	173	16.6	Sine Wave.....	197
	Construction.....	173		Sinusoidal Waveform	197
	Overload Protection.....	173		Nonsinusoidal Waveform.....	198
	Short-Circuit and Ground-Fault Protection	173	16.7	Nonsymmetrical Waveform.....	198
15.5	Circuit Breaker Trip Elements.....	173	16.8	Frequency	198
	Thermal Trip Element.....	173	16.9	Phase.....	198
	Magnetic Trip Element	173	16.10	Degrees	198
15.6	Circuit Breaker Types	174	16.11	Lead or Lag	199
	Inverse Time	174		Leading.....	199
	Adjustable-Trip.....	174		Lagging.....	199
	Instantaneous-Trip	174	16.12	Values of Alternating Current	199
15.7	Available Short-Circuit Current.....	174		Instantaneous	199
15.8	Interrupting Rating	175		Peak.....	199
15.9	Short-Circuit Current Rating.....	175		RMS.....	200
15.10	Current Limiting Protection	176	Unit 16 – Summary	201	
Part B – Ground-Fault Circuit Interrupters	176		Unit 16 – Conclusion	202	
15.11	How a GFCI Works	176	Unit 16 – Practice Questions	203	

Squirrel-Cage Induction Motor	251
Synchronous Motor	251
Wound-Rotor Motor	251
Universal Motor	252
20.15 Reversing the Rotation of an AC Motor	252
Unit 20 – Summary	253
Unit 20 – Conclusion	255
Unit 20 – Practice Questions	256
Unit 21 Generators	259
Introduction	259
21.1 Direct-Current Generator	259
Excitation Current	259
21.2 Alternating-Current Generator	260
21.3 Three-Phase Generators	260
21.4 Voltage Phase Relationship	261
Unit 21 – Summary	262
Unit 21 – Conclusion	262
Unit 21 – Practice Questions	263
Unit 22 Transformers	265
Introduction	265
22.1 Transformer Basics	265
Primary Versus Secondary	265
Mutual Induction	265
22.2 Secondary Induced Voltage	265
22.3 Autotransformers	266
Step Down	266
Step Up	266
22.4 Power Losses	267
Conductor Resistance Loss	267
Flux Leakage Loss	267
Eddy Currents	267
Hysteresis Losses	268
22.5 Harmonic Current	268
22.6 Efficiency	269
22.7 Transformer Turns' Ratio	269
22.8 Transformer kVA Rating	270
22.9 Current Flow	270
22.10 Current Rating	271
Unit 22 – Summary	273
Unit 22 – Conclusion	274
Unit 22 - Practice Questions	275
Chapter 6 – Final Review Questions	277
Final Practice Exam	281
Final Conclusion	295

Annex A Grounding and Bonding

Understanding the Basics of Electrical Systems	299
Understanding Electrical Shock Hazard	300
What Determines the Severity of Electrical Shock	301
Clearing a Ground Fault	302
Why Grounding is Often Difficult to Understand	302
250.1 Scope	305
250.2 Definitions	305
250.3 Other Code Sections	306
250.4 General Requirements for Grounding and Bonding	306
250.4(A) Summary	311
250.6 Objectionable (Neutral) Current	312