

# Table of Contents

## *Chapter 1 Electrical Theory .....* **1**

### *Unit 1 Electrician's Math and Basic Electrical Formulas.....* **3**

#### Part A – Electrician's Math .....

1–1	Fractions .....	3
1–2	Kilo .....	3
1–3	Knowing Your Answer .....	3
1–4	Multiplier .....	3
1–5	Parentheses .....	4
1–6	Percentages .....	4
1–7	Percent Increase .....	4
1–8	Percentage Reciprocals .....	5
1–9	Rounding .....	5
1–10	Squaring .....	5
1–11	Square Root .....	6

#### Part B – Basic Electrical Formulas..... **6**

1–12	Electrical Circuit .....	6
1–14	Power Source .....	6
1–15	Conductance and Resistance .....	7
1–16	Electrical Circuit Values .....	8
1–17	Ohm's Law $I = E/R$ .....	8
1–18	Pie Circle Formula .....	9
1–19	Formula Wheel .....	9
1–20	Power Changes with the Square of the Voltage .....	11

### *Unit 2 Electrical Circuits.....* **12**

#### Part A – Series Circuits..... **12**

##### Introduction to Series Circuits .....

2–1	Understanding Series Calculations .....	12
-----	---	----

#### Part B – Parallel Circuits .....

##### Introduction to Parallel Circuits .....

2–3	Practical Uses of Parallel Circuits .....	13
2–4	Understanding Parallel Calculations .....	14
2–5	Parallel Circuit Resistance Calculations .....	15
2–6	Parallel Circuit Summary .....	16

#### Part C – Series-Parallel and Multiwire Branch Circuits .....

##### Introduction to Series-Parallel Circuits .....

---

2-7	Review of Series and Parallel Circuits .....	16
2-8	Series-Parallel Circuit Resistance Calculations .....	17
Part D – Multiwire Branch Circuits.....		18
Introduction to Multiwire Branch Circuits .....		18
2-9	Neutral Current Calculations .....	18
2-10	Dangers of Multiwire Branch Circuit .....	19
<b>Unit 3 Understanding Alternating Current .....</b>		<b>22</b>
Part A – Alternating-Current Fundamentals.....		22
3-1	Current Flow .....	22
3-2	Alternating Current .....	22
3-3	Alternating-Current Generator.....	23
3-4	Waveform .....	23
3-5	Armature Turning Frequency .....	24
3-6	Phase – In and Out .....	24
3-7	Phase Differences in Degrees .....	24
3-8	Values of Alternating Current .....	25
Part B – Induction.....		25
Induction Introduction.....		25
3-9	Induced Voltage and Applied Current .....	26
3-10	Conductor Impedance .....	28
3-11	Induction and Conductor Shape .....	29
3-12	Induction and Magnetic Cores .....	29
Part C – Capacitance .....		31
Capacitance Introduction.....		31
3-13	Charge, Testing and Discharging .....	31
Part D – Power Factor and Efficiency .....		33
Power Factor Introduction.....		33
3-15	Apparent Power (Volt-Ampere).....	33
3-16	Power Factor .....	34
3-17	True Power (Watts) .....	35
3-18	Efficiency .....	38
<b>Unit 4 Motors and Transformers.....</b>		<b>42</b>
Part A – Motors.....		42
Motor Introduction .....		42
4-1	Motor Speed Control .....	43
4-2	Reversing a Direct-Current Motor .....	43
4-3	Alternating-Current Motors .....	43
4-4	Reversing Alternating-Current Motors .....	44
4-5	Motor Volt-Ampere Calculations .....	44
4-6	Motor Horsepower/Watts .....	46
4-7	Motor Nameplate Ampere .....	48
Part B – Transformer Basics.....		50
Transformer Introduction .....		50
4-8	Transformer Primary and Secondary .....	51

---

---

4-9	Transformer Secondary and Primary Voltage .....	51
4-10	Autotransformers.....	52
4-11	Transformer Power Losses.....	52
4-12	Transformer Turns Ratio .....	53
4-13	Transformer kVA Rating.....	53
4-14	Transformer Current .....	53

**Chapter 2 National Electrical Code Calculations.....57****Unit 5 Raceway, Outlet Box and Junction Box Calculations .....58**

5-1	Understanding the NEC, Chapter 9 .....	58
5-2	Raceway and Nipple Calculations .....	61
5-3	Existing Raceway Calculations.....	64
5-4	Tips For Raceway Calculations .....	65
Part B – Outlet Box Fill Calculations .....	65	
Introduction [314.16] .....	65	
5-5	Sizing Box – Conductors all the Same Size [Table 314.16(A)].....	66
5-6	Conductor Equivalents [314.16(B)].....	66
5-7	Sizing Box – Different Size Conductors [314.16(B)] .....	67
Part C – Pull, Junction Boxes, and Conduit Bodies.....	69	
Introduction.....	69	
5-8	Pull and Junction Box Size Calculations .....	69
5-9	Depth of Box and Conduit Body Sizing [314.28(A)(2), Ex.].....	70
5-10	Junction and Pull Box Sizing Tips .....	71

**Unit 6 Conductor Sizing and Protection Calculations.....72**

6-1	Conductor Insulation Property [Table 310.13].....	72
6-2	Conductor Allowable Ampacity [310.15] .....	72
6-3	Conductor Sizing [110.6] .....	73
6-4	Terminal Ratings [110.14(C)] .....	74
6-5	Conductors In Parallel [310.4] .....	74
6-6	Conductor Size – Voltage Drop [210.19(A) FPN 4 AWG and 215.2(A)(4) FPN 2].....	75
6-7	Overcurrent Protection [Article 240] .....	75
6-8	Overcurrent Protection of Conductors – General Requirements [240.4] .....	76
6-9	Overcurrent Protection of Conductors – Specific Requirements .....	77
6-10	Equipment Conductors Size and Protection Examples .....	78
Part B – Conductor Ampacity Calculations .....	81	
6-11	Conductor Ampacity [310.10] .....	81
6-12	Ambient Temperature Ampacity Adjustment Factor [Table 310.16] .....	81
6-13	Conductor Bundling Ampacity Adjustment Factor [Table 310.15(B)].....	82
6-14	Ambient Temperature and Conductor Bundling Adjustment Factors .....	83
6-15	Current-Carrying Conductors .....	84
6-16	Conductor Sizing Summary.....	85

---

<b>Unit 7 Motor Calculations.....</b>	<b>86</b>
Introduction.....	86
7-1 Motor Branch-Circuit Conductors [430.22(A)].....	86
7-2 Motor Overcurrent Protection.....	86
7-3 Overload Protection [430.32(A)] .....	87
7-4 Branch-Circuit Short-Circuit Ground-Fault Protection [430.52(C)(1)] ..	88
7-5 Feeder Conductor Size [430.24].....	89
7-6 Feeder Protection [430.62(A)] .....	90
7-7 Highest-Rated Motor [430.17].....	91
7-8 Motor Calculations Steps .....	91
7-9 Motor Calculation Review.....	92
7-10 Motor VA Calculations.....	94
<b>Unit 8 Voltage Drop Calculations.....</b>	<b>97</b>
Part A – Conductor Resistance Calculations.....	97
8-1 Conductor Resistance.....	97
8-2 Conductor Resistance – Direct-Current Circuits, [Chap. 9, Table 8] .....	99
8-3 Conductor Impedance – Alternating-Current Circuits.....	99
8-4 Alternating-Current Impedance as Compared to Direct-Current Resistance .....	99
8-5 Impedance [Chapter 9, Table 9 of the NEC] .....	100
Part B – Voltage-Drop Calculations .....	100
8-6 Voltage-Drop Considerations.....	100
8-7 NEC Voltage-Drop Recommendations .....	101
8-8 Determining Circuit Conductors Voltage Drop .....	101
8-9 Sizing Conductors to Prevent Excessive Voltage Drop .....	105
8-10 Limiting Conductor Length to Limit Voltage Drop .....	108
8-11 Limiting Current to Limit Voltage Drop .....	109
8-12 Extending Circuits.....	109
<b>Unit 9 Single Family Dwelling Unit Load Calculations.....</b>	<b>112</b>
Part A - General Requirements.....	112
9-1 General Requirements.....	112
9-2 Voltages [220.2(A)] .....	112
9-3 Fraction of an Ampere [220.2(B)] .....	112
9-4 Appliance (Small) Circuits [210.11(C)(1)] .....	112
9-5 Cooking Equipment – Branch Circuit [Table 220.19, Note 4].....	113
9-6 Laundry Receptacle(s) Circuit [210.11(C)(2)] .....	119
9-7 Lighting and Receptacles .....	119
Part B - Standard Method – Feeder/Service Load Calculations .....	120
9-8 Dwelling Unit Feeder/Service Load Calculations (Part II of Article 220).....	120
9-12 Neutral Calculations – General [220.22] .....	122

---

<b>Chapter 3 Advanced NEC Calculations .....</b>	<b>123</b>
<b>Unit 10 Multifamily Dwelling Units .....</b>	<b>124</b>
10-1 Multifamily Dwelling Unit Calculations – Standard Method .....	124
10-4 Multifamily Dwelling Unit Calculations [220.32] – Optional Method .....	125
10-5 Multifamily – Optional Method Example [220.32].....	128
<b>Unit 11 Commercial Load Calculations .....</b>	<b>129</b>
Part A – General.....	129
11-2 Conductor Ampacity [Article 100] .....	129
11-3 Conductor Overcurrent Protection [240.4] .....	129
11-4 Voltages [220.2(A)] .....	130
11-5 Rounding an Ampere [220.2(B)] .....	130
Part B – Loads .....	130
11-6 Air-Conditioning .....	130
11-7 Dryers .....	131
11-8 Electric Heat .....	131
11-9 Kitchen Equipment .....	131
11-11 Lighting – Demand Factors [Table 220.3(A) and 220.11] .....	133
11-12 Lighting Without Demand Factors [Table 220.3(A), 215.2(A)(1) and 230.42].....	134
11-13 Lighting – Miscellaneous .....	134
11-14 Multioutlet Receptacle Assembly [220.3(B)(8)] .....	134
11-15 Receptacles VA Load [220.13] .....	135
11-16 Banks and Offices – General Lighting and Receptacles .....	135
11-17 Signs [220.3(B)(6) and 600.5] .....	136
11-18 Neutral Calculations [220.22] .....	136
Part C – Load Calculation Examples .....	137
Marina [555.12].....	137
Mobile/Manufactured Home Park [550.31].....	137
Recreational Vehicle Park [551.73].....	138
Restaurant – Optional Method [220.36] .....	138
School – Optional Method [220.34] .....	140
<b>Unit 12 Delta/Delta and Delta/Wye Transformer Calculations .....</b>	<b>143</b>
12-1 Current Flow .....	152
Part A – Delta/Delta Transformers.....	152
12-2 Delta Transformer Voltage .....	152
12-3 Delta High-Leg.....	152
12-4 Delta Line Currents .....	153
12-5 Delta Phase Currents.....	153
12-6 Delta Phase versus Line Current.....	153
12-7 Delta Current Triangle.....	153
12-8 Delta Transformer Balancing .....	154
12-9 Delta Transformer Sizing .....	155
12-10 Delta Panel Balancing .....	155
12-11 Delta Panelboard and Conductor Sizing.....	155

---

---

12-12 Delta Neutral Current.....	155
12-13 Delta Maximum Unbalanced Load .....	156
Part B – Delta/Wye Transformers .....	156
12-15 Wye Transformer Voltage.....	156
12-16 Wye Voltage Triangle .....	156
12-17 Wye Transformers Current.....	157
12-18 Wye Line Current .....	157
12-19 Wye Phase Current .....	158
12-20 Wye Phase Versus Line Current .....	158
12-21 Wye Transformer Balancing .....	158
12-22 Wye Transformer Sizing.....	159
12-23 Wye Panel Balancing.....	159
12-24 Wye Panelboard and Conductor Sizing .....	159
12-25 Wye Neutral Current .....	160
12-26 Wye Maximum Unbalanced Load .....	160
12-27 Delta/Wye Example.....	160
12-28 Delta Versus Wye .....	160
<b>Index.....</b>	<b>162</b>